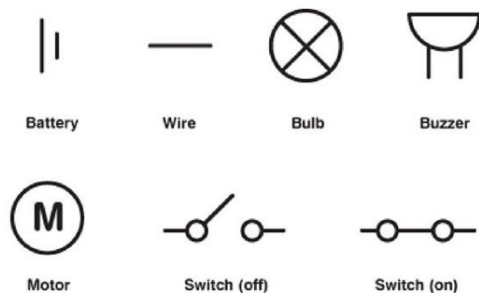
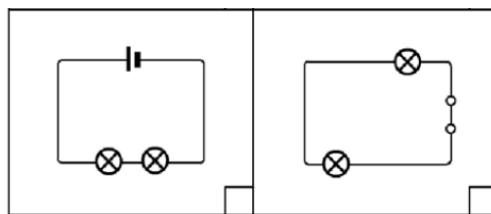


**Important Information****What are electrical circuit symbols?**

Electrical **components** are represented as **symbols** (pictures that stand for something else). We use them when drawing electrical circuit **diagrams**.

**Electrical Component Symbols****Circuit Diagrams**

- Draw the circuit symbols first.
- Use a ruler to draw the wires as straight lines and do not let them cross.

**Valuable Vocabulary**


<b>Bulb</b>	Provides light by passing an electrical current through a filament.
<b>Cell (battery)</b>	A stored source of electricity.
<b>Circuit</b>	A closed loop through which electricity can flow.
<b>Components</b>	Parts of an electric circuit e.g. battery, buzzer and bulb.
<b>Conductor</b>	An object that allows electricity to flow through it easily (metal is a good conductor).
<b>Insulator</b>	An object that does not allow electricity to flow through it easily e.g. plastic.
<b>Motor</b>	A machine that turns electrical energy into movement.
<b>Parallel circuit</b>	A circuit where the current is divided into separate paths.
<b>Resistance</b>	The difficulty electricity has when flowing around a circuit.
<b>Series circuit</b>	A circuit where all of the current flows through each part of the circuit.
<b>Switch</b>	A component that makes or breaks the connections in a circuit.
<b>Voltage</b>	A force that makes electricity flow through a wire.

**What is the effect of changing one component at a time in a circuit?**

- When switches are open or wires are removed (so it is **not a closed circuit**), bulbs, buzzers and motors will turn off.
- If you kept the number of batteries the same but added more bulbs and motors to a series circuit, they will be dimmer and slower. This is because the electricity is being shared between more components. More voltage would be needed to make them brighter.

**Voltage**

- More batteries (or a higher voltage) creates more power (or current) to flow through a circuit.

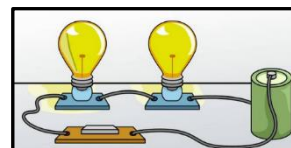**Top Takeaways**

- Recall parts of a circuit and their functions.
- Explain the impact of adding to, or removing components.
- Explore the effect of voltage on electrical circuit components.
- Build and create circuit models.
- Draw and annotate circuit diagrams.

### **Working scientifically (Science Skills)**

- i) Planning different types of scientific enquiries to answer questions, including recognising and controlling variables where necessary
- ii) Taking measurements, using a range of scientific equipment, with increasing accuracy and precision, taking repeat readings when appropriate
- iii) Recording results using scientific diagrams and labels
- iv) Using test results to make predictions to set up further comparative and fair tests
- v) Reporting and presenting findings from enquiries, including conclusions, causal relationships and explanations of and degree of trust in results